

**PIMPRI CHINCHWAD EDUCATION TRUST'S**  
**PIMPRI CHINCHWAD COLLEGE OF**  
**ENGINEERING SECTOR NO. 26, PRADHIKARAN,**  
**NIGDI, PUNE-44**



**DEPARTMENT OF ELECTRONICS AND**  
**TELECOMMUNICATION S.Y. (E&TC) 2023-24**  
**DIGITAL DESIGN USING VERILOG HDL**

**FORMATIVE ASSESSMENT - 2**

**Problem Statement**

Test Specification: Write a test bench to simulate the traffic light controller, verifying correct light sequences and state durations. Test various scenarios, including a reset condition and normal operation.

**Under the Guidance of Mrs. Deepti Khurge**  
**mam**

**NAME: Suyash Ghadage**  
**PRN NO: 122B1E054 ENTC A**

**1. Introduction :** A Finite State Machine (FSM) for Traffic Light Control in VHDL is a digital system designed to regulate the traffic signals at an intersection. The FSM operates by transitioning between different states that represent the lights: green, yellow, and red. Each state defines which light is active and for how long, ensuring smooth control of vehicle and pedestrian traffic.

## 2. Design Specification :

1. Design Specification : Design an FSM to control traffic lights at a simple intersection with two streets: Main Street (MS) and Side Street (SS).  
o States for each street: Green (G), Yellow (Y), and Red (R).  
o Light sequence for Main Street: Green → Yellow → Red.  
o Light sequence for Side Street: Red → Green → Yellow.  
→ Green → Yellow.

DDHU-FA

1. Problem Statement: Design Specification  
Design an FSM to control traffic lights at a simple intersection with two streets. Main Street: Green (G), Yellow (Y), & Red (R). Light sequence for side street: Red → Green → Yellow

→

Green (G) - vehicle can pass  
Yellow - vehicle should prepare to stop  
Red - vehicle must stop.

State - 1  
(MS) main street → Green → Yellow → Red  
(SS) Side street → Red → Green → Yellow

\* States of FSM:

State 1 MS = Green, SS = Red  
Transition after timer on main street expires (30 sec green)  
↓  
next - MS = Yellow, SS = Red  
State

State 2]:  
MS = Yellow, SS = Red  
Transition after timer on main street (5 sec yellow) ↓  
next - MS = Red, SS = Green  
State

PCCOE

State 3:

MS = Red , SS = Green

Transition after timer on SS expires  
(30 sec for green)

next MS = Red , SS = yellow  
state

State 4:

MS = red , SS = yellow

Transition after timer on SS expires  
next MS = Green , SS = Red.  
state

\* Assign digits to state.

MS = green , SS = red  $\rightarrow$  00

MS = green


MS = yellow , SS = red  $\rightarrow$  01

MS = red , SS = green  $\rightarrow$  10

MS = red , SS = yellow  $\rightarrow$  11



\* moore state diagram:

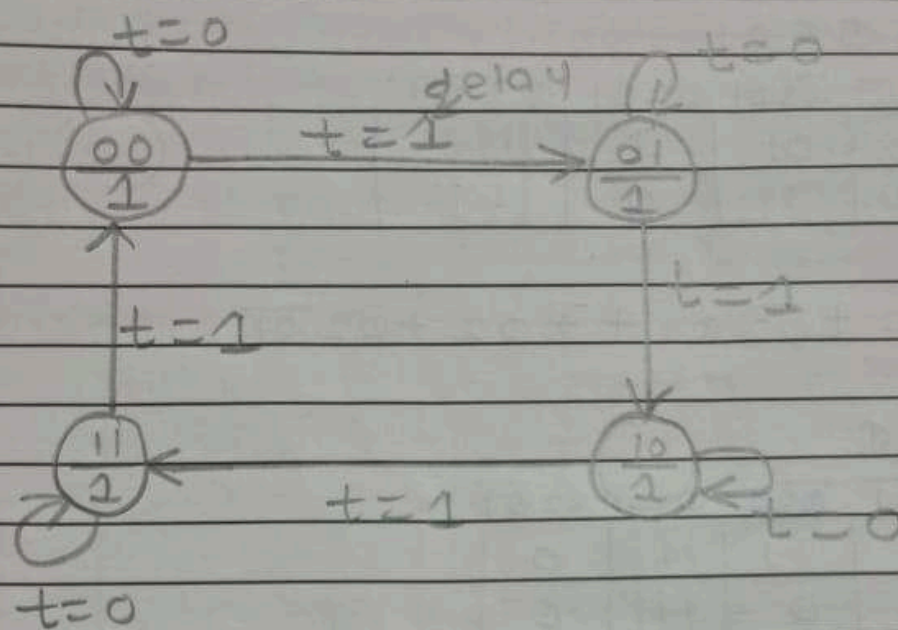

\* Truth table:

| $t$ | $Q_2$ | $Q_1$ | $Q_2^+$ | $Q_1^+$ | $D_2^+$ | $D_1^+$ | $y$ |
|-----|-------|-------|---------|---------|---------|---------|-----|
| 0   | 0     | 0     | 0       | 0       | 0       | 0       | 0   |
| 0   | 0     | 1     | 0       | 1       | 0       | 1       | 0   |
| 0   | 1     | 0     | 1       | 0       | 1       | 0       | 0   |
| 0   | 1     | 1     | 1       | 1       | 1       | 1       | 0   |
| 1   | 0     | 0     | 0       | 1       | 0       | 1       | 1   |
| 1   | 0     | 1     | 1       | 0       | 1       | 0       | 1   |
| 1   | 1     | 0     | 1       | 1       | 1       | 1       | 1   |
| 1   | 1     | 1     | 0       | 0       | 0       | 0       | 1   |

\* Kmap:

$$D_2^+ = Q$$

|                | $\overline{Q_2}\overline{Q_1}$ | $\overline{Q_2}Q_1$ | $Q_2\overline{Q_1}$ | $Q_2Q_1$ |
|----------------|--------------------------------|---------------------|---------------------|----------|
| $\overline{t}$ | 0                              | 0                   | 1                   | 1        |
| $t$            | 0                              | 1                   | 0                   | 1        |

$$D_2^+ = t\overline{Q_2}Q_1 + \overline{t}Q_2 + Q_2\overline{Q_1}$$

$$D_1^+ = Q$$

|                | $\overline{Q_2}\overline{Q_1}$ | $\overline{Q_2}Q_1$ | $Q_2\overline{Q_1}$ | $Q_2Q_1$ |
|----------------|--------------------------------|---------------------|---------------------|----------|
| $\overline{t}$ | 0                              | 1                   | 1                   | 0        |
| $t$            | 1                              | 0                   | 1                   | 0        |

$$D_1^+ = t\overline{Q_2}\overline{Q_1} + \overline{t}Q_1 + Q_2Q_1$$


$$Y = Q$$

|                | $\overline{Q_2}\overline{Q_1}$ | $\overline{Q_2}Q_1$ | $Q_2\overline{Q_1}$ | $Q_2Q_1$ |
|----------------|--------------------------------|---------------------|---------------------|----------|
| $\overline{t}$ | 0                              | 0                   | 0                   | 0        |
| $t$            | 1                              | 1                   | 1                   | 1        |

$$YQ = t$$



\* circuit diagram:

 

### 3. Test Bench:

We used a device from Artix-7 Family for this design.

Verilog Code Using Case Statement: Verilog Code Implementation: Implement the FSM in Verilog with inputs for the clock and reset signals. Outputs should indicate the state of the lights on Main Street and Side Street. Use parameters to define state durations (e.g., 10 clock cycles for green, 3 for yellow, 7 for red). A test bench to simulate the traffic light controller, verifying correct light sequences and state durations. Test various scenarios, including a reset condition and normal operation

Verilog code :module tb\_traffic\_light\_controller;

```
// Testbench signals
```

```
reg clk;
```

```
reg reset;
```

```
wire [1:0] main_street_light;
```

```
wire [1:0] side_street_light;
```

```
// Clock period
```

```
localparam CLK_PERIOD = 10;
```

```
// Instantiate the traffic light controller
```

```
traffic_light_controller uut (
```

```
    .clk(clk),
```

```
    .reset(reset),
```

```
    .main_street_light(main_street_light),
```

```
    .side_street_light(side_street_light)
```

```
);
```

```
// Clock generation
```

```
initial begin
```

```
    clk = 0;
```

```
    forever #(CLK_PERIOD / 2) clk = ~clk;
```

end

// Task to check light state and duration

task check\_state(input [1:0] expected\_main, input [1:0] expected\_side, input integer duration);

integer i;

for (i = 0; i < duration; i = i + 1) begin

    @(posedge clk);

    if (main\_street\_light !== expected\_main || side\_street\_light !== expected\_side) begin

        \$display("Error at time %t: Expected MS=%b, SS=%b, Got MS=%b, SS=%b",

                \$time, expected\_main, expected\_side, main\_street\_light, side\_street\_light);

    end

end

endtask

// Test procedure

initial begin

    // Apply reset

    \$display("Starting simulation...");

    reset = 1;

    @(posedge clk);

    reset = 0;

    // Test MAIN\_GREEN state

    \$display("Testing MAIN\_GREEN state (Main Street GREEN, Side Street RED)...");

    check\_state(2'b01, 2'b00, uut.MAIN\_GREEN\_DURATION);

    // Test MAIN\_YELLOW state

    \$display("Testing MAIN\_YELLOW state (Main Street YELLOW, Side Street RED)...");

    check\_state(2'b10, 2'b00, uut.MAIN\_YELLOW\_DURATION);



```
// Test SIDE_GREEN state

$display("Testing SIDE_GREEN state (Main Street RED, Side Street GREEN)...");
check_state(2'b00, 2'b01, uut.SIDE_GREEN_DURATION);


// Test SIDE_YELLOW state

$display("Testing SIDE_YELLOW state (Main Street RED, Side Street YELLOW)...");
check_state(2'b00, 2'b10, uut.SIDE_YELLOW_DURATION);


// Test reset functionality

$display("Testing reset...");
reset = 1;
@(posedge clk);
reset = 0;


// Verify reset to MAIN_GREEN state

check_state(2'b01, 2'b00, uut.MAIN_GREEN_DURATION);


$display("Simulation complete.");
$stop;
end

endmodule
```